

EE3006* Experiment-8 Lab Report

Putta Shravya - EE22B032
Polamuri Hasmatha - EE22B075
Vasireddy Yasaswi - EE22B040

October 2024

Power Measurement

A Digital wattmeter uses an ADC (Analog-to-Digital Converter) to digitize the voltage (or scaled down version of the voltage) across the load. It employs another ADC to simultaneously digitize another voltage signal that is proportional to the load current. A schematic of such an arrangement is shown in Fig. 1. The sampling frequency has to be sufficiently high, to reproduce the signal accurately in the digital domain. To compute the active power P , an average of the product of the samples of the ADC outputs is used. For this computation equation (1) can be used. In equation (1), N indicates the number of samples in a complete cycle. In the circuit given in Fig. 1, a small resistor R_s is connected in series with load. It acts as the current sensing resistor. The output v_o of the Op-Amp OA (OP07) is given by (). The voltage v_{in} (VI) is taken as the voltage across the load. The voltages v_{in} and v_o can be sampled using an NI ELVIS board. The power across the load can be computed from the acquired signals using a LABVIEW Virtual Instrument (VI), by building an appropriate program that realizes equation (1).

$$P = \frac{1}{N} \sum_{j=1}^N v_{Lj} \cdot i_{Lj}$$

Figure 1: Lock-in amplifier

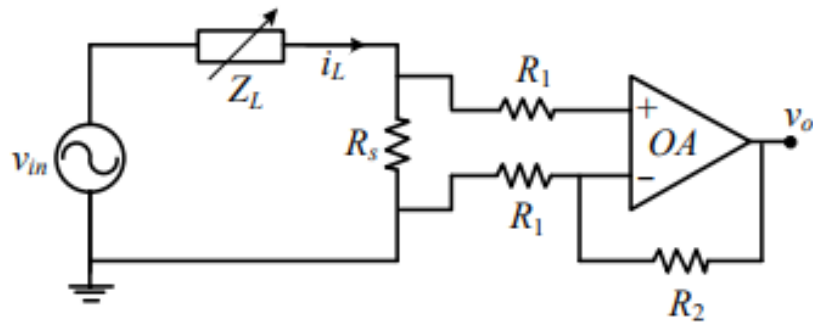


Fig1. Power measurement circuit

Expected

$R_s = 1 \text{ ohm}$
 $R_1 = 3 \text{ kohm}$
 $R_2 = 120 \text{ kohm}$
 $R = Z_L = 51 \text{ ohm}$

Pexpected = 0.2494

Actual

$R_s = 1.6 \text{ ohm}$

$R_1 = 3 \text{ kohm}$

$R_2 = 119.5 \text{ kohm}$

$R = Z_L = 50.4 \text{ ohm}$

$P_{\text{measured}} = 0.2601$

Absolute error = 4.29%

Now adjusting the value of R_s such that error in measurement is within 1%, then we get
 $P_{\text{measured}} = 0.2471$

New Absolute error = 0.922%

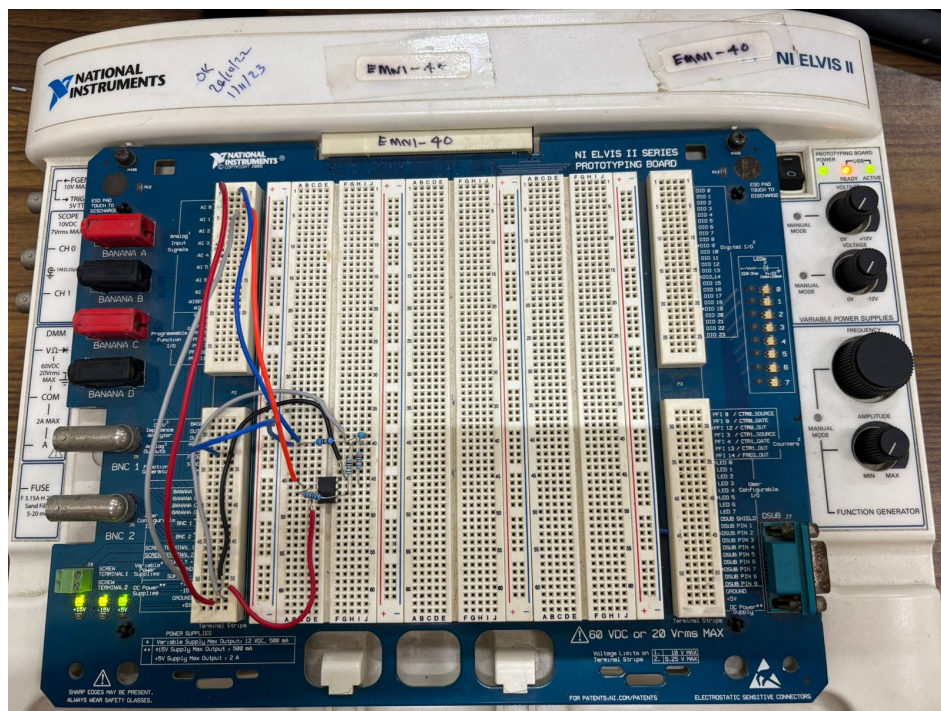


Figure 2: Elvis Board

Z_L	P at 50Hz	P at 100Hz	P at 200Hz
$R = 51$	0.255	0.256	0.262
$R = 100$	0.222	0.226	0.223
$C = 25 \text{ uF}$	0.001	0.003	0.047
$R = 51 \text{ in series with } C = 25 \text{ uF}$	0.081	0.109	0.224
$R = 100 \text{ in series with } C = 25 \text{ uF}$	0.125	0.167	0.192

Table 1: 6x4 Table Example

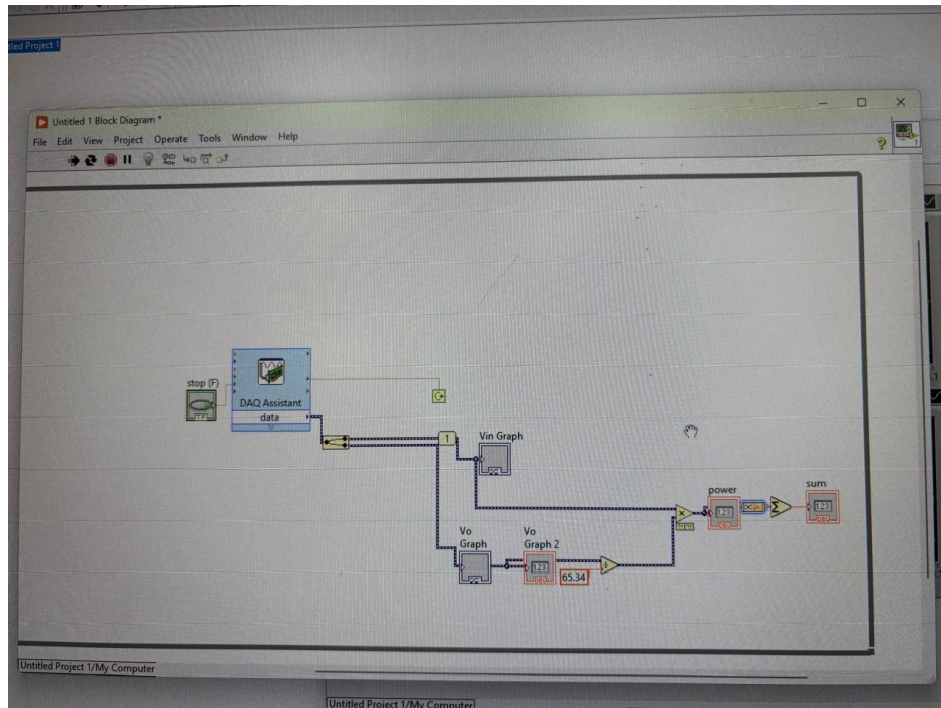


Figure 3: LABView

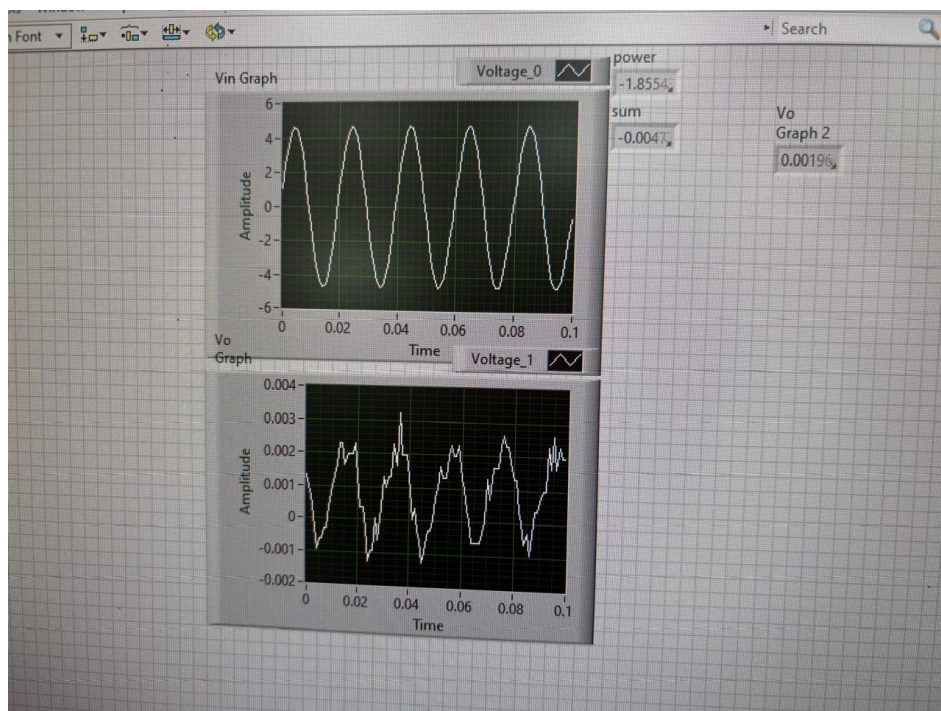


Figure 4: V and I Graphs